

Lab Exercises

Buck Chopper:

1. Power up the IGBT chopper/inverter & DAC modules.
2. Make sure the DAC module is USB connected to the PC.
3. Open LVDAC-EMS and ensure that the data acquisition and control the IGBT chopper/inverter modules are checked. Then hit "OK."
4. Select Tools >> Chopper/Inverter Control.
5. Set the function to Buck Chopper (high side switching).
6. Using Q1 (on the IGBT chopper/inverter module) as the electronic switch, connect the necessary components for a buck chopper with a 300 Ω resistive load.
7. Using the LVDAC-EMS scope and metering, set up to monitor the voltage difference between Q1's gate and emitter (V_{GE}) (from "switching control input 1" to the white ground terminal on the chopper), source voltage, and load voltage. Use the metering function to observe the average of each voltages and the oscilloscope function to observe each voltage instantaneously.
 - a. Make sure you turn on "continuous refresh" in both the scope and metering windows.
 - b. Make sure that the voltmeters you use are set to DC.
8. Using the DC power supply, apply 20V to the input of the chopper.
9. Pick your favorite switching frequency for the chopper and press start
10. Change the duty cycle and observe what happens. Using sketches or screenshots, show the relationship between the gating signal (V_{GE}) and the output voltage.


11. Record a few average output voltages for different duty cycles.

a. Does the equation you had in the pre-lab match your results?

12. Keeping the duty cycle constant and vary the switching frequency. How does frequency affect the output voltage?

Boost Chopper

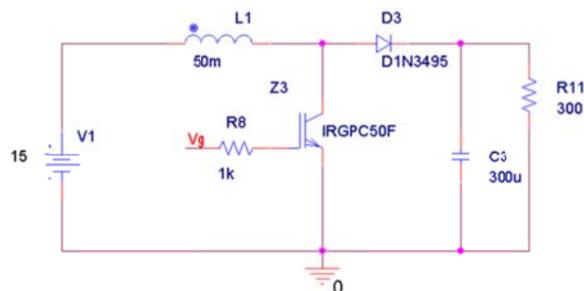1. Change over to a boost chopper. Use the 50 mH filtering inductor. The cap will be the built-in C_{bus} . Use the same 300 Ω load and a **15 Vdc** source.



2. In addition to the voltages you monitored for the buck chopper, monitor the inductor current and voltage (average and scope) and the load current.

3. Start up the power supply and the chopper and play with the duty cycle. **Don't let the duty cycle exceed 75%**. See what happens to output voltage.

a. Why don't we want to run the boost chopper at high duty cycles?

Name:


Time:

- a. Use the graph function of the data table to make plots of V_{out} vs. D and Efficiency vs. D.
Note: When using the graph function always plot "Points and Curves."

- b. Comment on your findings.

Boost Chopper w/ PV array

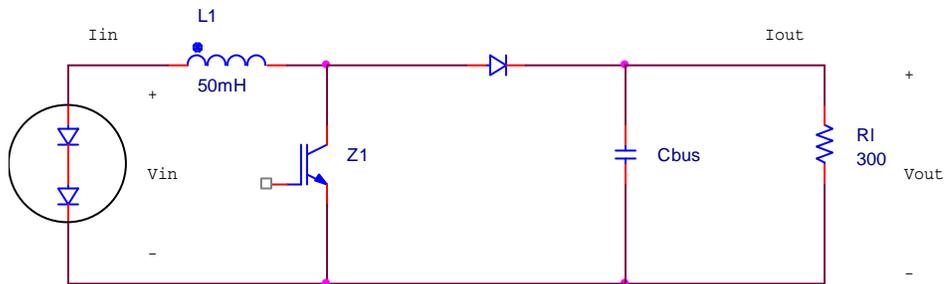1. Leave the boost chopper connections in place, but this time instead of a 15 Vdc source, use a solar panel with a work light as the input.



2. Use the worklight distances you used last week when finding curves. Therefore one of your curves should be a good predictor for how this panel will behave. Use your curve to predict the maximum power point voltage.
3. Make the same measurements as in the last part (V_{in} , V_{out} , I_{in} , I_{out} , P_{in} , P_{out} , efficiency, and duty cycle). Present them as a table.
 - a. How good was your estimate of maximum power point voltage?

