

Grid connection requirements: IEEE 1547-2003 standard provides rules for connecting distributed resources to the grid, such as if one wanted to put solar panels on one's roof. The standard can be downloaded from IEEE Xplore.

1. List 3 requirements for connecting distributed resources to the grid.

Filtering: The equation for instantaneous output voltage of a single phase full bridge inverter (VSI) is:

$$v_o = \sum_{n=1,3,5\dots}^{\infty} \frac{4V_s}{n\pi} \sin(n\omega t)$$

v_o is an infinite sum of sinusoids of whose frequencies are integer multiples of the fundamental, w . We say that the voltage contribution from the $n=1$ sinusoid is the fundamental. All other voltage contributions we collectively refer to as harmonics. For example, the 3rd harmonic is described as: $\frac{4V_s}{3\pi} \sin(3\omega t)$. If the fundamental is 60 Hz, as in the US, the 3rd harmonic will be 180 Hz and so on.

Generally, harmonics are a bad thing in an electric power system; they lead to problems with equipment and increased losses. Therefore, we want to minimize them as much as possible. As you might have seen when doing the previous problem, IEEE 1547 provides rules for the amount of THD allowed when connecting distributed resources to the grid. Total harmonic distortion is defined as

$= \frac{1}{I_1} (\sum_{n=2,3\dots}^{\infty} I_n^2)^{1/2}$. $TDD = \text{total demand distortion} = THD \frac{\text{fundamental load current}}{\text{circuit rating}}$. We'll deal with THD only in this lab. One way to reduce the THD of an inverter is to use a filter.

1. What type of filter would be best to use?

Name:

Time:

Lab Exercises

Voltage source inverters

1. Implement a single-phase, 180° modulation, full-bridge VSI. Use a DC source as the input; you choose the voltage. Use any resistive load you like, just be sure not to exceed its ratings. Be sure the toggle switches on the IGBT Chopper/Inverter module are in their correct positions.
2. Take screenshots of the output voltage and current waveforms. Note when each transistor is on.

3. Do the diodes ever conduct? Why or why not?

Filtering

1. Run the inverter with a 20 V DC source as the input and a $17\ \Omega$ resistor as a load. Take a screenshot of the harmonic analyzer for the output current and note the THD (the Labvolt software calls it merely “distortion”).

